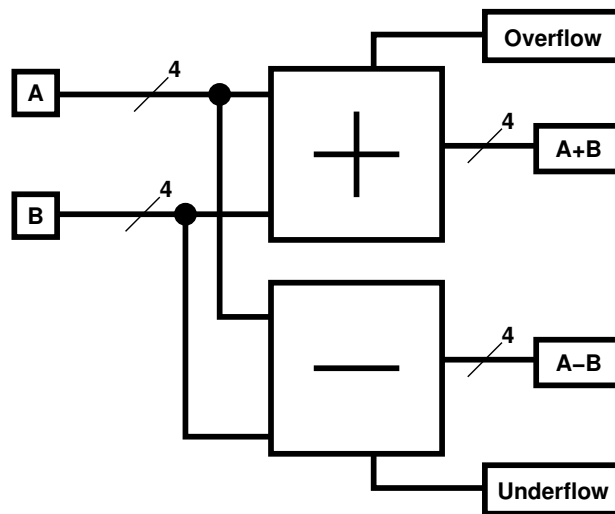


## A 4-bit Adder/Subtractor and a Sequential Circuit

---



You are given an 8-input, 10-output circuit.  $A$  and  $B$  are numbers encoded in natural binary, using 4 bits:  $A_3, A_2, A_1, A_0$  and  $B_3, B_2, B_1, B_0$ .

The outputs are also encoded in natural binary and defined as follows:

$A+B = (P_3, P_2, P_1, P_0)$  and  $A-B = (M_3, M_2, M_1, M_0)$ .

Finally, the overflow  $O$  and the underflow  $U$  outputs indicate occurrence of exceeding capacity. Your task is to design a gate-level schematic of the circuit.


### Questions:

1. Draw a truth table of the adder.

We would **never** manage to draw a truth table with  $2^8 = 256$  rows!

We shall use the *divide-and-conquer* method instead:


The “division” phase:

 


The first phase of the “conquest”:

Prob.1:	$A_0$	$B_0$	$r_0$	$P_0$	$r_0$	$B_0$	$P_0$	$B_0$
	0	0	0	0	$A_0$	$\begin{array}{ c c } \hline 0 & 0 \\ \hline 0 & 1 \\ \hline \end{array}$	$A_0$	$\begin{array}{ c c } \hline 0 & 1 \\ \hline 1 & 0 \\ \hline \end{array}$
	0	1	0	1	$r_0 = A_0 \cdot B_0$			
	1	0	0	1	$P_0 = A_0 \oplus B_0$			
	1	1	1	0				
Prob.2: Prob.3: Prob.4:	$r_{n-1}$	$A_n$	$B_n$	$r_n$	$P_n$	$r_n$	$B_n$	
	0	0	0	0	0	$A_n$	$\begin{array}{ c c c c } \hline 0 & 0 & 1 & 0 \\ \hline 0 & 1 & 1 & 1 \\ \hline \end{array}$	
	0	0	1	0	1	$r_{n-1}$		
	0	1	0	0	1	$P_n$	$B_n$	
	0	1	1	1	0	$A_n$	$\begin{array}{ c c c c } \hline 0 & 1 & 0 & 1 \\ \hline 1 & 0 & 1 & 0 \\ \hline \end{array}$	
	1	0	0	0	1	$r_{n-1}$		
	1	0	1	1	0	$r_n = A_n \cdot B_n + r_{n-1} \cdot A_n +$		
	1	1	0	1	0	$r_{n-1} \cdot B_n$		
	1	1	1	1	1	$P_n = A_n \oplus B_n \oplus r_{n-1}$		

The second phase of the “conquest”:

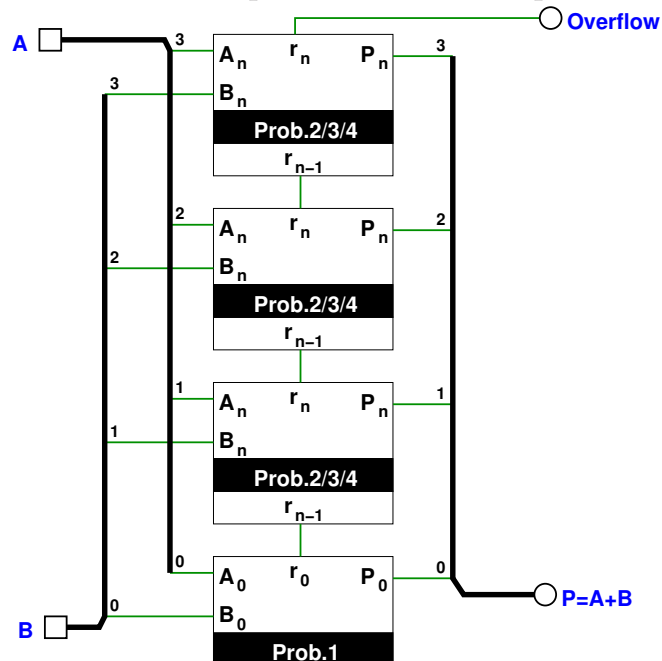

Alternative:

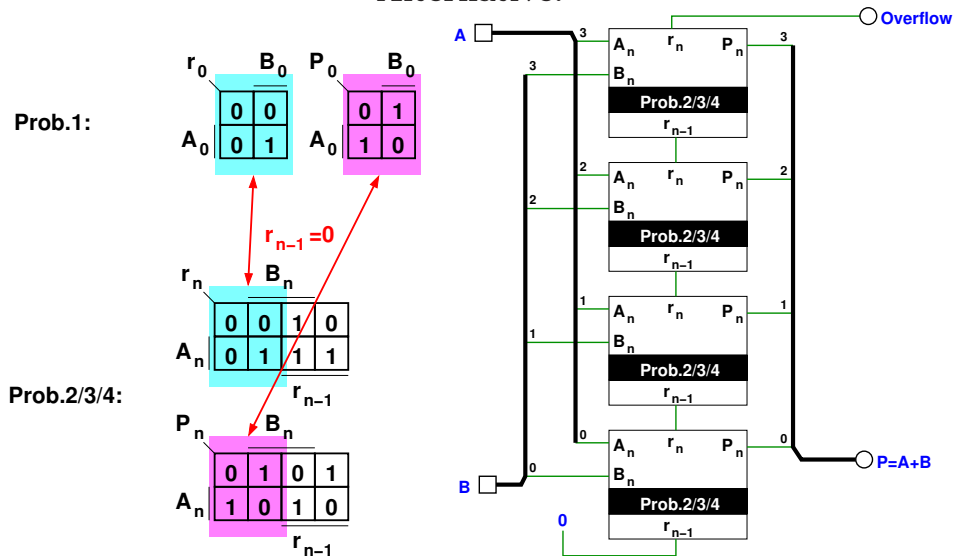


- Using Logisim, design and verify a gate-level schematic of the adder.

See the logisim file.

- Draw a truth table of the subtractor.

Again we use the *divide-and-conquer* method:


The “division” phase:

 

The first phase of the “conquest”:

Prob.5:	$A_0$	$B_0$	$e_0$	$M_0$	$e_0$	$B_0$	$M_0$	$B_0$
	0	0	0	0	$A_0$	$\begin{array}{ c c } \hline 0 & 1 \\ \hline 0 & 0 \\ \hline \end{array}$	$A_0$	$\begin{array}{ c c } \hline 0 & 1 \\ \hline 1 & 0 \\ \hline \end{array}$
	0	1	1	1	$e_0 = \overline{A_0} \cdot B_0$			
	1	0	0	1	$M_0 = A_0 \oplus B_0$			
	1	1	0	0				
Prob.6: Prob.7: Prob.8:	$e_{n-1}$	$A_n$	$B_n$	$e_n$	$M_n$	$e_n$	$B_n$	
	0	0	0	0	0	$A_n$	$\begin{array}{ c c c c } \hline 0 & 1 & 1 & 1 \\ \hline 0 & 0 & 1 & 0 \\ \hline \end{array}$	
	0	0	1	1	1	$e_{n-1}$		
	0	1	0	0	1	$M_n$	$B_n$	
	0	1	1	0	0	$A_n$	$\begin{array}{ c c c c } \hline 0 & 1 & 0 & 1 \\ \hline 1 & 0 & 1 & 0 \\ \hline \end{array}$	
	1	0	0	1	1	$e_n = \overline{A_n} \cdot B_n + e_{n-1} \cdot \overline{A_n} +$		
	1	0	1	1	0	$e_{n-1} \cdot B_n$		
	1	1	0	0	0	$M_n = A_n \oplus B_n \oplus e_{n-1}$		
	1	1	1	1	1			


The second phase of the “conquest”:

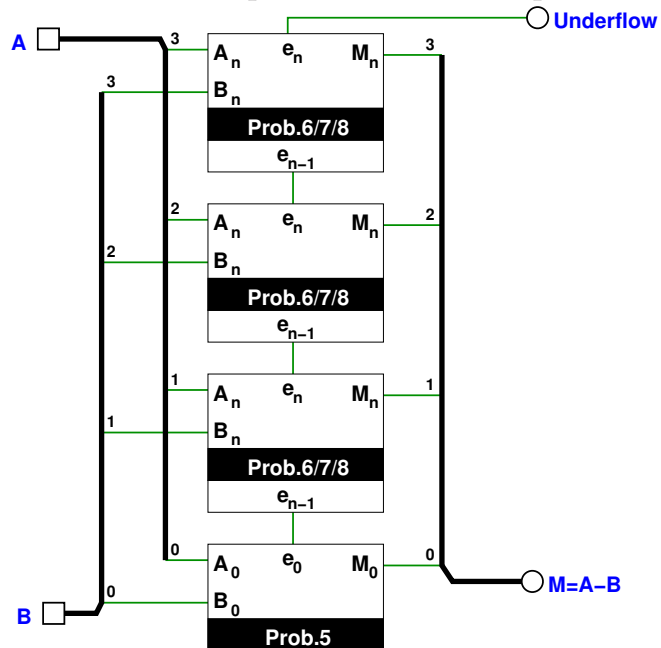

## A 4-bit Adder/Subtractor and a Sequential Circuit

---

Alternative:

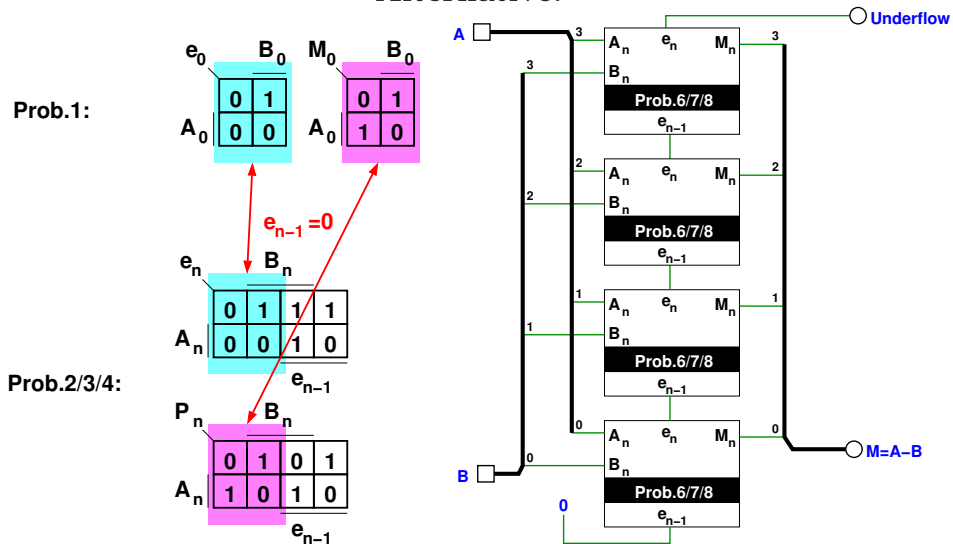

4. Using Logisim, design and verify a gate-level schematic of the subtractor.


See the logisim file.

---
 
## A 4-bit Adder/Subtractor and a Sequential Circuit

---

The purpose of this exercise is to design a controller circuit for a three-light-system. The state of the three lights changes on each press or release of the button, according to the scheme below:



Tasks to complete:


- Implement a system with the described functionality in Logisim. You are only allowed to use simple logic gates, SR-latches, LEDs, and buttons.

For each LED, we have one SR-latch. Let us recall the functionality of an SR-latch:

Set	Reset	function
0	0	Keeping the prior state
0	1	LED off
1	0	LED on

We can now observe the behavior of a single LED:
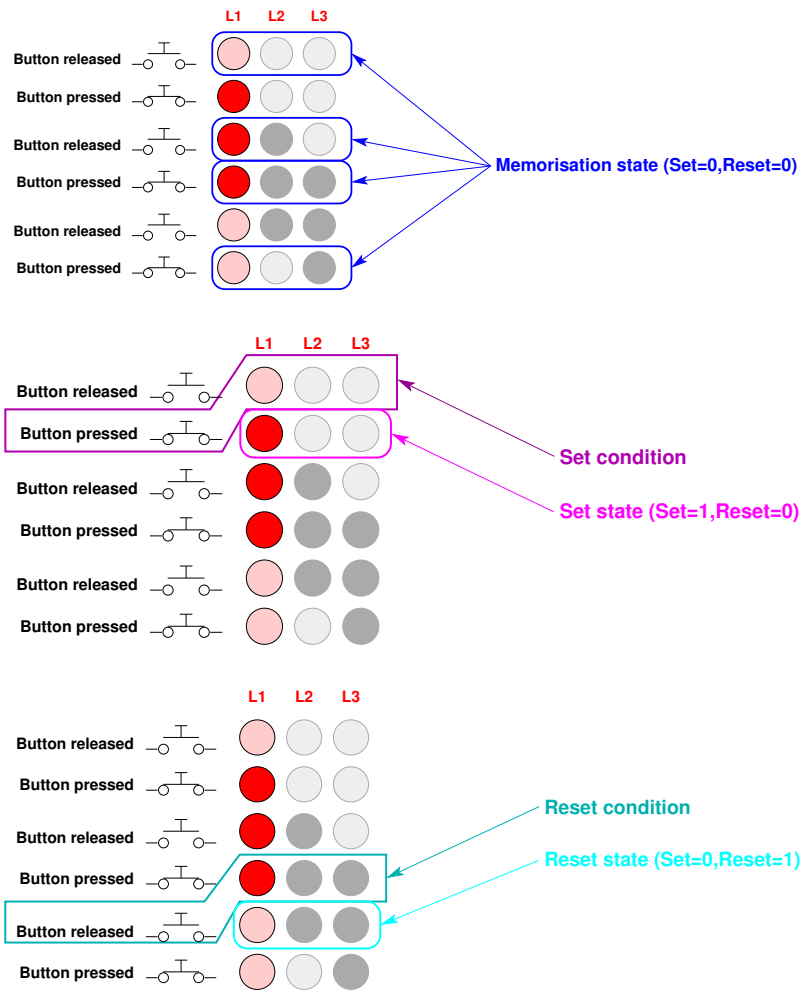
## A 4-bit Adder/Subtractor and a Sequential Circuit



The states and transition conditions need to be determined for all three LEDs. For the solution, see the logisim file.

- Download your design to the GECKO4Education board. What do you observe?